Exp 2: Design of Common Source Amplifier with Negative Feedback Bias





