
Exp 7: Amplifier Design with Current Mirror Bias

```
        --- Operating Point ---

V(n001):        5               voltage
V(n002):        1.9128          voltage
I(R1):          0.0030872       device_current
I(V):           -0.00910683     device_current
Ix(u1:1):       0.00601962      subckt_current
Ix(u1:2):       1.61742e-09     subckt_current
Ix(u1:3):       -0.00601962     subckt_current
Ix(u2:1):       0.0030872       subckt_current
Ix(u2:2):       1.61742e-09     subckt_current
Ix(u2:3):       -0.0030872      subckt_current
```

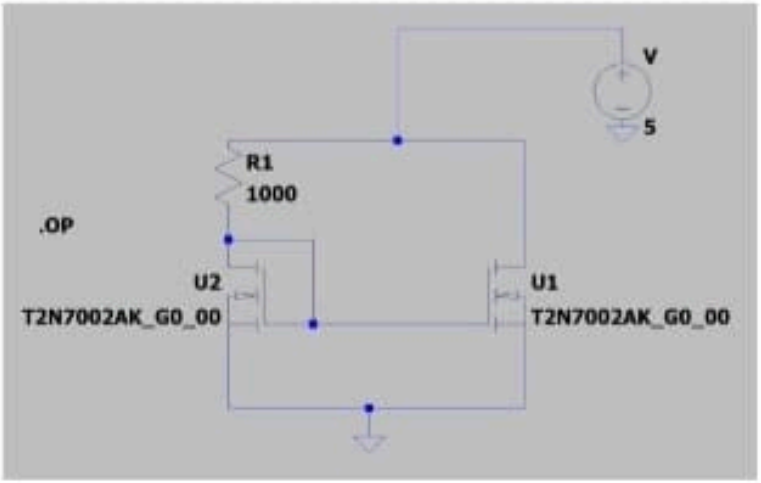


```
Note: No compatibility mode selected!

Circuit: * mosfet current mirror experiment

Doing analysis at TEMP = 27.000000 and TNOM = 27.000000

Using SPARSE 1.3 as Direct Linear Solver

No. of Data Rows : 1
v(drain1) = 2.101550e+00
v(drain2) = 5.000000e+00
i(v1) = -5.79690e-03
i(v2) = -2.89845e-03
ngspice 3 ->
```

